 


03 Logic networks

03.03 Sequential circuits

- Dealing with feedback
- Finite state machines
- Latches
- Flip flops
- Registers
- Synchronous sequential circuits

Dealing with feedback



s	r	y	y'
0	0	?	?
0	1	0	1
1	0	1	0
1	1	0	0


s	r	y	y'	y	y'
0	0	0	0	1	1
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1		

Sequential circuits: FSMs

- Finite state machines (FSM): (S, I, O, f, g, s_0)
 - Output function $o=f(s,i)$
 - Next-state function $s^{next}=g(s,i)$
 - Representation: state diagram
- Classification:
 - Combinational $f:I \rightarrow O$
 - Sequential (Mealy's) $f:S \times I \rightarrow O$ $g:S \times I \rightarrow S$
 - Sequential (Moore's) $f:S \rightarrow O$ $g:S \times I \rightarrow S$
- Asynchronous vs Synchronous

Moore's FSM: example

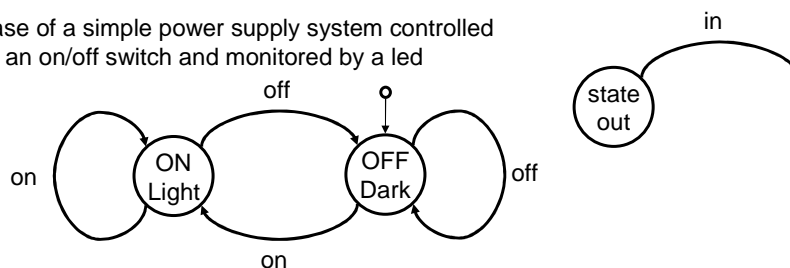Case of a simple power supply system controlled by an on/off switch and monitored by a led




$S = \{ON, OFF\}$
 $I = \{on, off\}$
 $O = \{Light, Dark\}$

$f: S \rightarrow O$
 $g: S \times I \rightarrow S$

State	Input	f Output	g Snext
OFF	off	Dark	OFF
OFF	on	Dark	ON
ON	off	Light	OFF
ON	on	Light	ON

Mealy's FSM: example

 
Case of a simple power supply system controlled by an on/off switch and monitored by a led when a test button is pressed



S = {ON,OFF}
I = {on,off,test}
O = {Light,Dark}
f: SxI → O
g: SxI → S


State	Input	f Output	g Snext
OFF	off	Dark	OFF
OFF	on	Dark	ON
OFF	test	Dark	OFF
ON	off	Dark	OFF
ON	on	Dark	ON
ON	test	Light	ON

FSMs: example

 

state	input (sr)	f	g
A	00	01	A
A	01	01	A
A	10	10	B
A	11	00	A
B	00	10	B
B	01	01	A
B	10	10	B
B	11	00	B

Latch SR

 


			y	y'
y'	s	r	f	g
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

RESET (rows 1-4)
HOLD (rows 5-6)
SET (rows 7-8)

In order to use the circuit to store a bit, we need three input configurations to:

- set $y=1$ regardless of the current state
- set $y=0$ regardless of the current state
- keep y unchanged

Latch SR

 


			y	y'
y'	s	r	f	g
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

RESET (rows 1-4)
HOLD (rows 5-6)
SET (rows 7-8)

- $(s,r) = (1,0)$ SET
- $(s,r) = (0,1)$ RESET
- $(s,r) = (0,0)$ HOLD
- $(s,r) = (1,1)$ NOT ALLOWED


Notice that $y' = \text{NOT } y$ for all allowed input configurations

Flip Flop SR

 


Clk	S	R	s	r	
0	0	0	0	0	HOLD
0	0	1	0	0	HOLD
0	1	0	0	0	HOLD
0	1	1	0	0	HOLD
1	0	0	0	0	HOLD
1	0	1	0	1	RESET
1	1	0	1	0	SET
1	1	1	1	1	NOT ALLOWED

Flip Flop D Level Sensitive

 


Clk	D	S	R	s	r	
0	0	0	1	0	0	HOLD
0	1	1	0	0	0	HOLD
1	0	0	1	0	1	RESET
1	1	1	0	1	0	SET


Flip Flop D Edge Triggered

 


Flip Flop D edge triggered

 

Registers

 

Flip Flop D edge triggered

 

Synchronous Sequential Circuits

