

03 Logic networks

03.05 Digital systems

- RTL representation
- Data path and Control unit
- Project styles
- Examples
- Data transfers among registers
- BUS and Address

Register-Transfer Level (RTL)


- Building blocks:
 - Registers
 - Functional macros
 - Steering logic
 - Finite state machines
- Data path
 - Functional part of the design composed of registers, functional macros and steering logic (interconnections and multiplexers)
- Control unit
 - FSM that generates the control bits for the multiplexers of the data path

Project styles

1. Single-stage network (e.g., RCAn)
 - Computation requires a single clock cycle
2. N-stage network (e.g., SRCAn)
 - Computation requires N clock cycles
 - Stages may be balanced or unbalance
3. Pipelining (e.g., PRCAn)
 - A new computation is started every clock cycle independetly of the latency
4. Resource sharing (e.g., BSAAn)
 - The same functional macro is used to perform different operations in different clock cycles



Example

- $F=a*b+c$

 

  Example

• $F = x_1 * c_1 + x_2 * c_2 + x_3 * c_3$






$$T_c = T_c(\text{MUL}) + T_c(\text{ADD})$$

$$T_p = T_c(\text{MUL}) + 2T_p(\text{ADD})$$

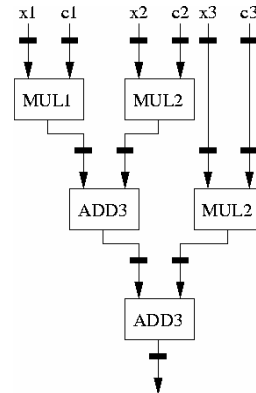  Example

• $F = x_1 * c_1 + x_2 * c_2 + x_3 * c_3$





2-stage network has lower latency than
3-stage network iff $T_p(\text{ADD}) < \frac{3}{4} T_p(\text{MUL})$

2-stage network has higher throughput than
3-stage network iff $T_p(\text{ADD}) < \frac{1}{2} T_p(\text{MUL})$

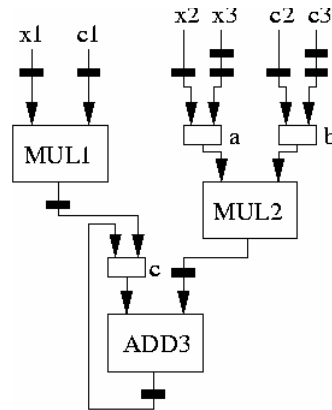 Example

• $F = x1 \cdot c1 + x2 \cdot c2 + x3 \cdot c3$



Resource sharing:
Use 2 multipliers to perform 3 products
Use 1 adder to perform 2 sums


Control unit

clock cycle	a	b	c
0	0	0	--
1	1	1	1
2	--	--	0

clock cycle	a	b	c
00	0	0	--
01	1	1	1
10	--	--	0

clock cycle	control	state	control	next state
00	0	00	0	01
01	1	01	1	10
10	0	10	0	00

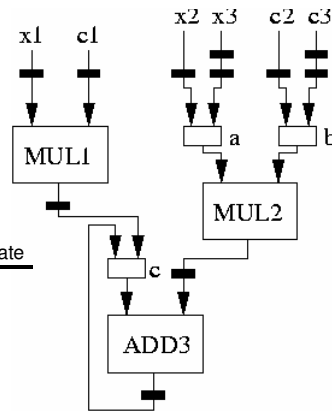control = s_0
 $s_0^{next} = s_0' s_1'$
 $s_1^{next} = s_0$




Data transfer among registers (BUS)


Shared communication channel (BUS)

Issues:

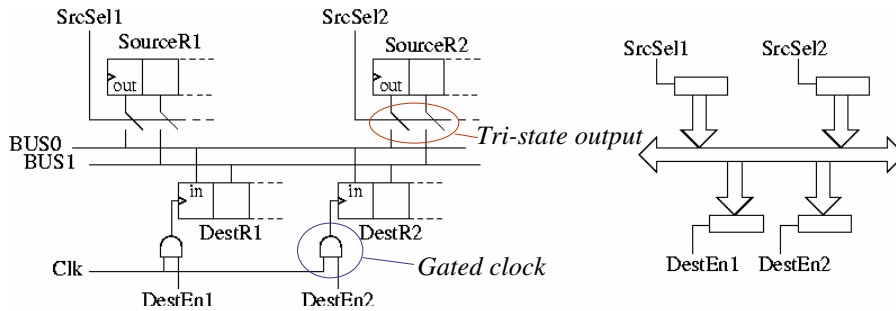- Select a single (*source*) register at the time to drive the BUS
- Enable a single (*destination*) register at the time to get data from the BUS



Data transfer among registers (BUS)

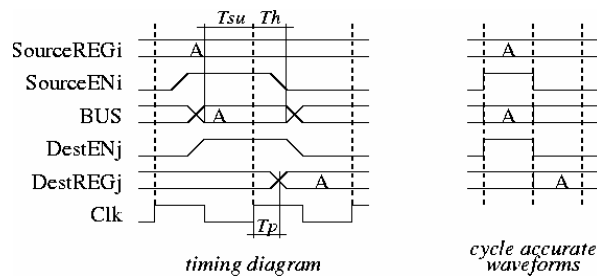

Addressing

